

LINEARIZING HIGH POWER AMPLIFIERS



Allen Katz
Linearizer Technology, Inc.

REV. B : 09.13.04

ABSTRACT


New communications services have created a demand for highly linear high power amplifiers (HPAs). This paper discusses the use of linearization for improving HPA linearity. Different methods of linearization are introduced and compared. The linearization of solid state power amplifiers (SSPAs), traveling wave tube amplifiers (TWTAs) and klystron power amplifiers (KPAs) is considered. Predistortion is shown to be the preferred linearization approach for many applications.

INTRODUCTION

Technological developments are rapidly changing the communication business. In the past, the bulk of satellite transmissions were single carrier video signals. Digital compression now allows many television signals to be transmitted in the frequency space previously occupied by a single signal. Non-video, multiple signal VSAT (very small aperture terminals) and mobile telephone/internet services are altering traditional

satellite loading. New terrestrial microwave services for the transmission of video, data, cellular telephone and personal communications are appearing daily. Bandwidth efficient modulation (BEM) schemes are becoming common. Virtually all these services involve the transmission of multiple signals and/or large quantities of information at high data rates. For such signals, whether transmitted by frequency division multiple access (FDMA), code division multiple access (CDMA) or time division multiple access (TDMA), amplifier linearity is a major consideration.

At high power levels (>100 watts) TWTAs and KPAs offer the best microwave performance in terms of size, cost and efficiency, but lag behind SSPAs in linearity. The use of linearization can yield TWTA and KPA performance comparable or superior to conventional SSPAs. At lower powers the advantage switches to SSPAs. As a result of new stringent linearity requirements, even relatively linear SSPAs can benefit from linearization.

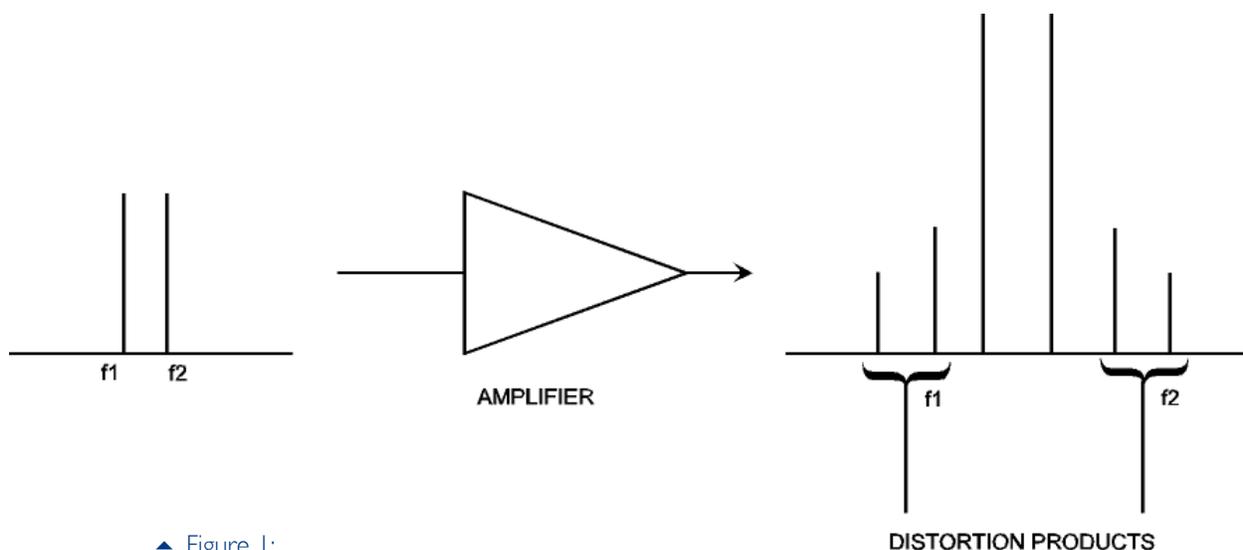

▲ Figure 1:
When 2 signals are amplified, distortion products appear in the vicinity of the desired signals.

NEED FOR LINEARITY

Distortion can be thought of as the creation of undesired signal energy at frequencies not contained in the original signal. Distortion is produced by a loss of linearity. Amplitude linearity can be considered a measure of how closely the input-output transfer response of an amplifier resembles a straight-line. When an amplifier's input level increases by a certain percent, its output level should increase by the same percent. A deviation from a straight-line can be represented by a power series.

$$V_{out} = K_1 V_{in} + K_2 V_{in}^2 + K_3 V_{in}^3 + \dots + K_n V_{in}^n \quad (1)$$

When a single carrier input signal, represented by a sine wave, is substituted into this expression the output waveform will contain the original sine wave and harmonic distortion products. The harmonics can be eliminated by filtering and do not pose a problem except for wideband communications applications of an octave or greater bandwidth. However, when more than one carrier is present, beat products are produced in the vicinity of the input signals. These new signals are known as intermodulation distortion (IMD) products. They are located at frequencies above and below the input carriers, and at frequency intervals equal to the separations of the input carriers. This is illustrated in Figure 1. Filtering cannot easily eliminate IMD products since they are located on the same frequency or near to the desired input signals.

Distortion is also produced by phase non-linearity. The shift in phase angle that a signal encounters in passing through an amplifier is a measure of the time delay. Ideally this phase shift, or time delay, should be constant for all power levels.

$$\theta(P) = \text{constant}, \quad (2)$$

In practical amplifiers, there can be a substantial change in phase with power level.

$$\theta = f(P_{in}). \quad (3)$$


This change in phase with amplitude converts variations in signal level to phase modulation. For a sinusoidal signal envelope,

$$P_{in}(t) = k(A \cos[\omega_m t])^2,$$

the resulting spectrum resembles that of a sinusoidal modulated PM signal, where ω_c is the carrier frequency, ω_m is the modulation frequency and M is the modulation index.

$$A_c \cos(\omega_c t + M \cos[\omega_m t]) = A_c \sum_{n=-\infty}^{n=\infty} (M)^n \cos([\omega_c + n\omega_m]t), \quad (4)$$

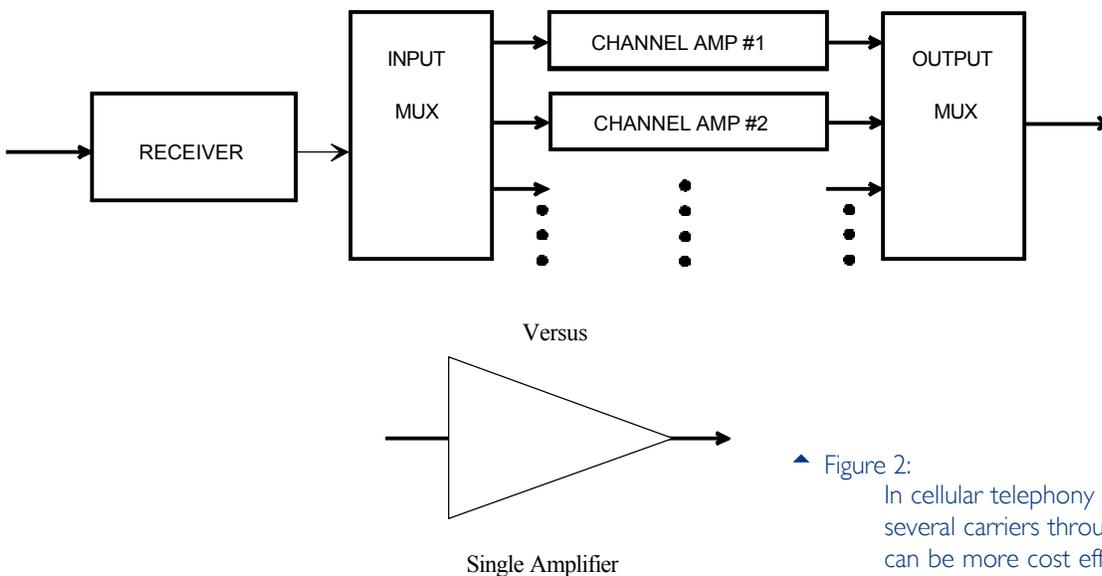where ω_c is the carrier frequency, ω_m is the modulation frequency (frequency of the envelope), and M is the modulation index (proportional to A). The PM sidebands are the IMD. Thus phase non-linearity produces IMD products in a similar fashion to amplitude non-linearity. In some systems phase non-linearity is the principal cause of distortion.



▲ Figure 2: In cellular telephony sending several carriers through one amplifier can be more cost effective.

When multiple signals are sent through a communications system, an amplifier must be operated at a reduced power level (backed-off) in order to keep distortion at an acceptable level. Distortion is often measured as the ratio of carrier - to - IMD power level. This ratio is know as C/I. An acceptable IMD level usually depends on the carrier-to-noise ratio (CNR) required at the receiver. IMD products are considered to add to a receiver's noise level on a power basis. For a carrier to IMD ratio:

- if C/I=CNR, the resultant CNR degrades by approx. 3 dB
- if C/I=CNR+6 dB, the resultant CNR degrades by approx. 1dB
- if C/I=CNR+ 10 dB, the resultant CNR degrades by approx. 0.5 dB

Thus, if the IMD products are to have a small affect on system preformance, they should be at least 10 db smaller than the carrier level. In the case of cellular telephony, it is often more convenient and cost effective to transmit several carriers through a common amplifier rather than to use multiple amplifiers and a lossy multiplexer, as is illustrated in Figure 2. To avoid unacceptably high IMD the common amplifier must be highly linear.

For the transmission of a single carrier, IMD is usually not a limitation. However with digitally modulated signals, spectral regrowth (SR) can be a serious problem, and manifests itself in a form equivalent to IMD. SR is not unique to digital signals, but an aspect of angle modulation (FM and PM). Angle modulated signals have a theoretically infinite bandwidth; for example, the spectrum of a sinusoidal modulated PM signal of equation (3) contains an infinite number of sidebands. In practice the bandwidth is limited to a finite frequency band, beyond which sideband amplitude drops off rapidly. Analog PM has an approximate bandwidth given by Carson's rule.

$$BW=2(\Delta f+f_m), \tag{5}$$

where Δf is the peak deviation and f_m is the modulation frequency. The effective bandwidth of angle modulated digital signals can be much greater than predicted by equation (5), due to the high frequency components of the modulating waveform. To reduce their bandwidth to a more acceptable value, digital waveforms are normally low-pass filtered before modulation. Because of the mechanics of most digital modulators, which are not true angle modulators, the amplitude of the carrier is also modulated by this process. In addition any "band limiting" filtering of an angle-modulated signal will introduce amplitude modulation. It is primarily this incidental amplitude modulation, which causes the SR when a digital signal is passed through a non-linear amplifier. The distortion of the induced amplitude waveform produces IMD products, which increase the signal's spectrum.

The change in phase with amplitude (3) converts the variations in signal level to angle modulation sidebands. These new sidebands further broaden the signal bandwidth. Amplitude and phase induced spectral products add as vectors and are classified in general as IMD.

SR is a major concern in personal communications since transmission often occurs on a channel adjacent to one in which reception of a much weaker distant signal may be taking place. To ensure freedom from interference, transmitter IMD products must be below the carrier (C/I ratio) by anywhere from 35 to greater than 65 dB, depending on the application.

The summation of the IMD terms in the adjacent channel is referred to as the adjacent channel power (ACPR).

$$ACPR = \Sigma IMDs \text{ | in the adjacent channel.}$$

These levels of linearity are considerably higher than had been required of communications amplifiers in the past, except for some special applications.

Saturated Power

All amplifiers have some maximum output power capacity, referred to as saturated power or simply saturation (SAT) - see Figure 3. Driving an amplifier with a greater input signal will not produce an output above this level. As an amplifier is driven closer to SAT, its deviation from a straight-line response will increase. Its output level will increase by a smaller amount, for a fixed increase in input signal as shown in Figure 3. Thus the closer an amplifier is driven to SAT, the greater the amount of distortion it produces.

The SAT point of TWTAs and KPAs is clearly defined as the output power normally decreases beyond SAT. Many SSPAs are sensitive to overdrive and can be easily damaged by operation at or beyond SAT. In addition, SSPAs tend to approach saturation exponentially. These factors make engineers reluctant to measure and use saturated power as a reference for comparison of SSPA performance. They prefer to use the power at which an amplifier's gain compresses by 1 dB as the reference (REF) for amplifier comparison.

$$REF=1-dBCP-SAT - D. \tag{6}$$

For SSPAs with reasonable linearity, the difference (D) in output level between SAT and the 1 dB compression point (CP) is about 1 dB. Unfortunately D varies from amplifier to amplifier. Generally amplifiers with high linearity will have a smaller difference (D < .25 dB), while amplifiers with poor linearity can have a difference of several dB (D > 2 dB).

For this reason, in this paper the relative amplifier performance will be referenced to (single carrier) saturated power. Output power backoff (OPBO) will be relative to an amplifier's single carrier saturated power. (For most SSPAs, SAT can be safely determined using a network analyzer in a rapid power sweep mode. For amplifiers that are especially thermally sensitive, pulsed power sweep techniques may be used.) When comparing the data presented here with that of SSPAs based on a 1 dB CP reference, an appropriate correction factor should be assumed.


Generally an HPA's greatest efficiency will occur at or near SAT. Similarly the closer to SAT a linear amplifier, (class A and to a large extent class AB), is driven, the greater the amount of distortion produced. For a satellite system, if a CNR of 16 dB (10 dB FM threshold + 6 dB for rain fading) is required and the IMD products are to have a negligible effect, then a C/I ≥ 26 dB is needed. To satisfy this requirement a TWTA would typically have to be backed off 5 to 7 dB, and sometimes more. This is about a 4 to 1 reduction in usable power. For TDMA applications the back-off is less, usually 2 to 4 dB, to keep distortion in the form of SR from interfering with adjacent channel communications. To satisfy cellular/PCS adjacent channel IMD requirements, a (class A) SSPA typically has to be backed-off about 6.5 dB for a C/I = 35 dB and sometimes by more than 15 dB for a C/I > 65 dB. These are huge reductions in usable output power. Therefore it is desirable to look at various linearization techniques

Linearization is a systematic procedure for reducing an amplifier's distortion. There are many different ways of linearizing an amplifier. Usually extra components are added to the design of a conventional amplifier. Often these extra components can be configured into a subassembly or box that is referred to as a linearizer. Linearization allows an amplifier to produce more output power and operate at a higher level of efficiency for a given level of distortion. Feed-forward, Feedback and Predistortion are some common forms of linearization. Besides these, there are a variety of other approaches that are being investigated. Most of these approaches use special techniques to obtain a linear output signal, from highly nonlinear amplifiers. None of these alternate methods widely applied in wireless or microwave applications.


Feed-Forward Linearization

Feed-forward (FF) has been extensively used with SSPAs, and functions well with TWTAs and KPAs, but is rather complex to implement, and not easily added to an existing amplifier. A block diagram of a basic FF system is shown in Figure 4. This system consists of two loops. The first loop subtracts samples of the input signal (Sin) from the output signal (Sout1) to produce a sample of the main amplifier's distortion. Sout1 consists of the amplified input signal plus any distortion introduced by the amplifier.
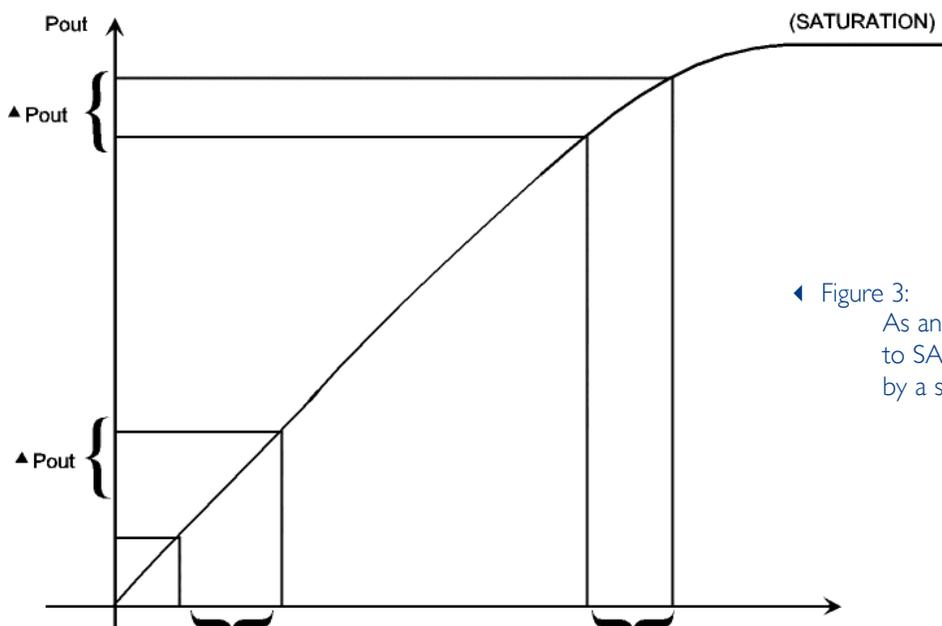
$$S_{out1} = GS_{in} \angle \Phi_{amp} + IMD, \tag{7}$$



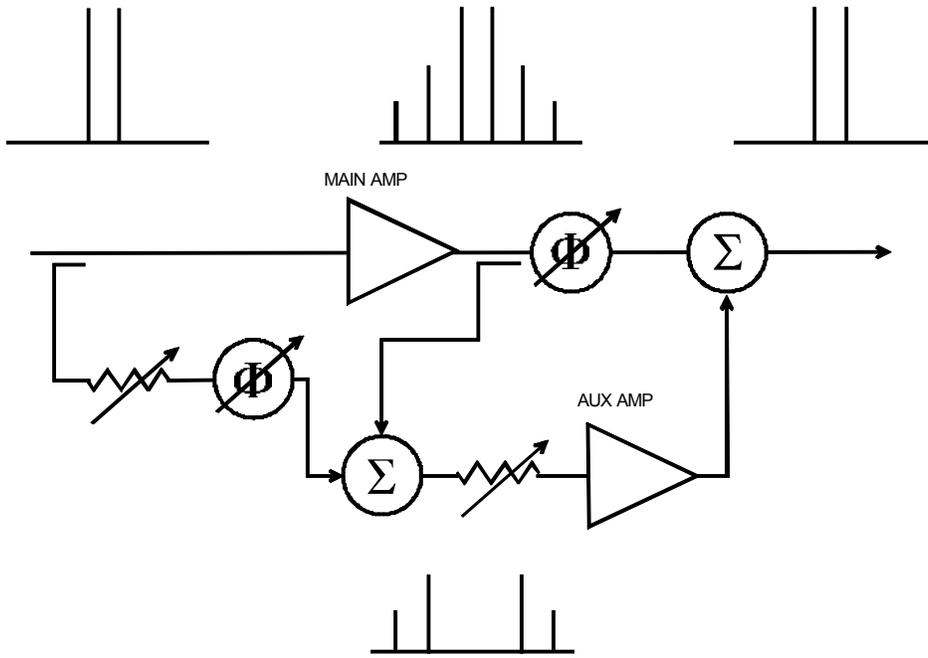◀ Figure 3:
As an amplifier is driven closer to SAT, its output level will increase by a smaller amount



◀ Figure 4:
Feed-forward linearization
employs 2 loops for the
cancellation of IMD.

where G is the gain and $\angle\Phi_{amp}$ is the phase shift introduced by the main amplifier. The samples of S_{in} (SS_{in}) and S_{out1} (SS_{out1}) are respectively

$$SS_{in} = K_0 S_{in} \quad \text{and} \quad SS_{out1} = K_1 S_{out1}$$

where K_0 and K_1 are the coupling coefficients of the directional couplers used to sample S_{in} and S_{out1} respectively. If SS_{in} is attenuated and delayed in phase such that

$$A_0 SS_{in} \angle\Phi_0 = -SS_{out1} \quad \text{or}$$

$$A_0 K_0 S_{in} \angle\Phi_0 = G K_1 S_{in} \angle(\Phi_{amp} + 180^\circ), \quad (8)$$

then S_{in} is canceled and the output of loop 1 is $K_1 \text{IMD}$. A_0 and Φ_0 are respectively the attenuation and phase shift introduced in loop 1 for adjustment of the carrier cancellation.

The second loop subtracts the amplified sampled distortion of loop 1 from a delayed S_{out1} to produce **ideally** a distortion free output signal (S_{out2}). The loop 1 output signal is amplified by an auxiliary (aux) amplifier of gain G_A and phase shift Φ_{aux} to provide a correction signal (S_{cor}) of sufficient level to cancel the distortion introduced by the main amplifier. S_{cor} is combined with the main amplifier signal at a final directional coupler of coefficient K_2 . If

$$S_{cor} = A_1 G A K_2 \text{IMD} \angle(\Phi_{aux} + \Phi_1) = \text{IMD} \angle(\Phi_m + 180^\circ) \quad (9)$$

then the HPA output will be distortion free. A_1 and Φ_1 are respectively the attenuation and phase shift introduced in loop 2 for adjustment of the distortion cancellation. Φ_m is a delay added after the main amplifier to equalize the delay introduced by the aux amplifier.

$$S_{out2} = S_{out1} \angle\Phi_m + S_{cor} \quad (10)$$

From this discussion it may appear that undistorted output can be obtained from a FF amplifier right up to SAT. Saturated output power can never be obtained from a FF amplifier because of the losses in the phase shifter and couplers, which must be located after the main amplifier. The main signal, S_{out1} , is reduced in amplitude by a factor (R_1) due to passing through the K_1 coupler. In dB

$$R_1 = 10 \log(1 - 10^{-(K_1/10)}) + L_1, \quad (11)$$

where L_1 is the dissipation loss of the coupler in dB. K_1 can be made very small, provided the main amplifier has sufficient gain. (A K_1 of -30 dB is not unusual). The K_2 of the final directional coupler must also be relatively small to minimize the loss of output power (R_2). Since the two signals, (carriers and distortion), being combined are not at the same frequency, power will be split between the load and the coupler's dump port. The R_2 power loss in dB as function of K_2 is described by equation (11) with 2 substituted for 1 in the variable names. The overall loss in saturated power ΔSAT is

$$10\text{Log}(1-10^{-(k1/10)})+10\text{Log}(1-10^{-(k2/10)})+L_1+L_2+L_m, \quad (12)$$


where L_m is the loss of the delay line (Φ_m). In practice it is very difficult to achieve a ΔSAT of less than 1 dB. ΔSAT can be considered the minimum OPBO of a FF amplifier. In actuality, ΔSAT must be added to the difference between the saturated power of an amplifier with single and multi-carrier signals. This factor can vary from about .5 to >1.5 dB for HPAs. Furthermore, the amplifier's **true** SAT power should not be considered only the power from the main amplifier. A FF amplifier combines both the power of the main and the aux amplifier. The sum of the saturated power of both these amplifiers should be considered when comparing the relative OPBO performance of different methods of linearization.

Practical considerations limit the size of the aux amplifier. This limits S_{COR} and, in turn, the undistorted FF output level. The smaller K_2 is set, the larger in power the aux amplifier must be sized. The aux amplifier must also be operated relatively linear so as not to **distort** the distortion signal, and thus introduce distortion of its own. Figure 5 shows the relationship between minimum OPBO (referenced from single carrier SAT of the main amplifier and the aux amplifier) and aux amplifier size (relative to the main power amplifier) for cancellation of IMD. Minimum OPBO is given for different values of output

coupler coefficient K_2 . These results depend on the linearity of the main and aux amplifiers and on the resistive loss of the couplers and delay line. Linear characteristics typical of a class A GaAs FET SSPA were assumed for both amplifiers, and resistive losses of 1 dB were assumed for the passive output components. Figure 5 shows that with an aux amplifier of half the size of the main amplifier (3 dB), cancellation of IMD can be achieved only up to about -6.3 dB from SAT with a K_2 of 6 dB. If only the saturated power of the main amplifier is considered, the minimum **corrected** OPBO is -4.2 dB, but occurs for an aux amplifier equal in size to the main amplifier and a K_2 of about 3 dB. (A minimum IMD cancellation of 20 dB was assumed. If only 10 dB is acceptable, an additional 1 to 2 dB increase in output level can be achieved.) In practice other factors limit IMD reduction and perfect cancellation can never be achieved. Figures 5 reveals why FF is not a good choice for linearization of amplifiers near SAT. Other linearization methods can provide superior IMD cancellation with considerably less complexity. However for OPBOs greater than ~ 6 -7 dB, FF becomes competitive, and for high linearity may be the system of choice.

Feedback Linearization

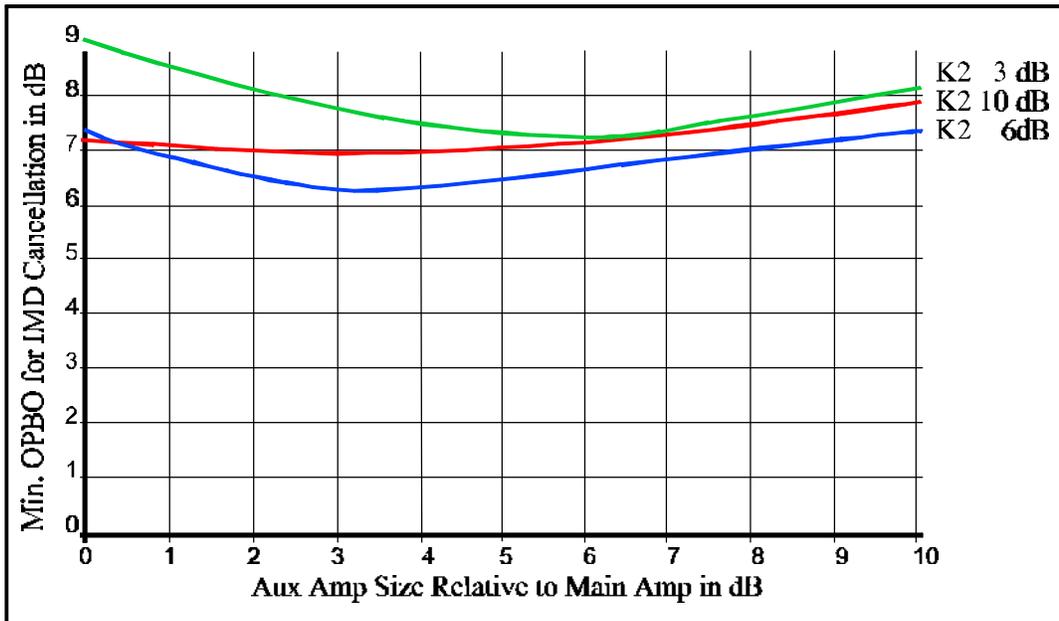There has been considerable work on the use of feedback for the linearization of RF and microwave amplifiers. Feedback



▲ Figure 5:
The minimum OPBO for cancellation of IMD by a FF amplifier depends on aux amplifier size and output coupler coefficient

comparison to produce an indirect form of FF linearization. Superior linearity can be obtained by correcting both amplitude and phase. The magnitude and phase error signals can be determined as illustrated in Figure 6. The resulting voltages are used to control an attenuator and a phase shifter to minimize signal error.

An alternate approach, known as Cartesian feedback, separates the signal into in-phase and quadrature components. This eliminates the need for phase-shift components and still allows the correction of gain and phase by adjusting the amplitudes of two orthogonal components. Figure 7 shows an example of Cartesian-feed-back system. The baseband in-phase and quadrature components are compared and used to control the attenuators in a vector modulator. Detection must be done synchronously (quadrature detection).

Cartesian feedback is most often used with quadrature phase-shift-keyed (QPSK) modulation. In this case, the output-side demodulated in-phase and quadrature components are subtracted directly from the respective in-phase quadrature modulation signals at the input. This eliminates the need to demodulate on the input side. The correction at baseband is often done in the digital domain using digital signal processing (DSP) techniques.

Very high linearity can be achieved by using IFB, which is self-correcting for changes due to environmental and aging effects. IFB's principal limitation is an inability to handle wideband signals. In practice, it is difficult to make a feedback system respond to signal envelope changes much greater than several MHz, because of the delay (Δt_s) of the amplifier and associated signal-processing components. The signal bandwidth must satisfy.

$$BW < 1/(4\Delta t_s) \quad (14)$$

for significant correction. Thus the total delay must be less than 25 ns for a 10 MHz bandwidth. Microwave amplifiers can have delays of 10 to 20 ns. An advantage of Cartesian feedback is that the BWs of the in-phase and quadrature components are approximately equal, while in Polar feedback systems, the BW of the phase component is much greater than the BW of the amplitude component.

Predistortion Linearization

Predistortion (PD) linearizers have been used extensively in microwave and satellite applications because of their relative simplicity, and their ability to be added to existing amplifiers as separate stand alone units. Unlike FF linearizers they can pro-

vide a viable improvement in linearity near SAT, but can be difficult to apply in applications requiring very high linearity ($C/I > 50$ dB). PD linearizers generate a non-linear transfer characteristic, which is the reverse of the amplifier's transfer characteristics in both magnitude and phase as seen in Figure 8. An alternate way of thinking of a PD linearizer is to view the linearizer as a generator of IMD products. If the IMDs produced by the linearizer are made equal in amplitude and 180 degrees out phase with the IMDs generated by the amplifier, the IMDs will cancel. This condition occurs when the gain and phase of the linearized amplifier remain constant with change in power level.

In dB, the gain of the linearizer (GL) must increase by the same amount the amplifier's gain (GA) decreases.

$$GL(P_{outL}) - GL_{ss} = -[GA(P_{inA}) - GA_{ss}] \quad | \quad P_{outL} = P_{inA}, \quad (15)$$

where GL_{ss} and GA_{ss} are respectively the small signal gains of the linearizer and the amplifier, and $GL(P_{outL})$ and $GA(P_{inA})$ are respectively these gains as a function of linearizer output and amplifier input levels. Likewise, the phase shift introduced by the linearizer must increase by the same amount the amplifier's phase decreases, (or vice-versa depending on the direction of phase change by the amplifier).

$$\Phi L(P_{outL}) - \Phi L_{ss} = -[\Phi A(P_{inA}) - \Phi A_{ss}] \quad | \quad P_{outL} = P_{inA}. \quad (16)$$

When these conditions are met, the result is the composite linear transfer characteristic shown in Figure 8. This is the response of a so called **ideal limiter**. Once an amplifier has saturated, it is impossible to obtain more output power by driving the amplifier harder. Thus the best a PD linearizer can do is to produce an **ideal limiter** characteristic. Despite this limitation, it is possible for a linearizer to provide large benefits in signal quality when output power is reduced from saturation. Some improvement is possible even at SAT and beyond as the linearizer can correct for post-saturation phase distortion and power slump - but this improvement is usually very small. Since the power out of the amplifier (in dB) is

$$P_{outA} = P_{inA} + GA = P_{outL} + GA = P_{inL} + GL + GA.$$


Equations (15) and (16) can be rewritten referenced to the power into the linearizer (P_{inL}), and the desired transfer characteristics of the linearizer expressed as follows:

$$GL(P_{inL}) = GL_{ss} + GA_{ss} - GA(P_{inL} + GL(P_{inL})) \quad (17)$$

$$\Phi L(P_{inL}) = \Phi L_{ss} + \Phi A_{ss} - \Phi A(P_{inL} + GL(P_{inL})). \quad (18)$$

Equations (16) and (17) can be solved iteratively for the ideal

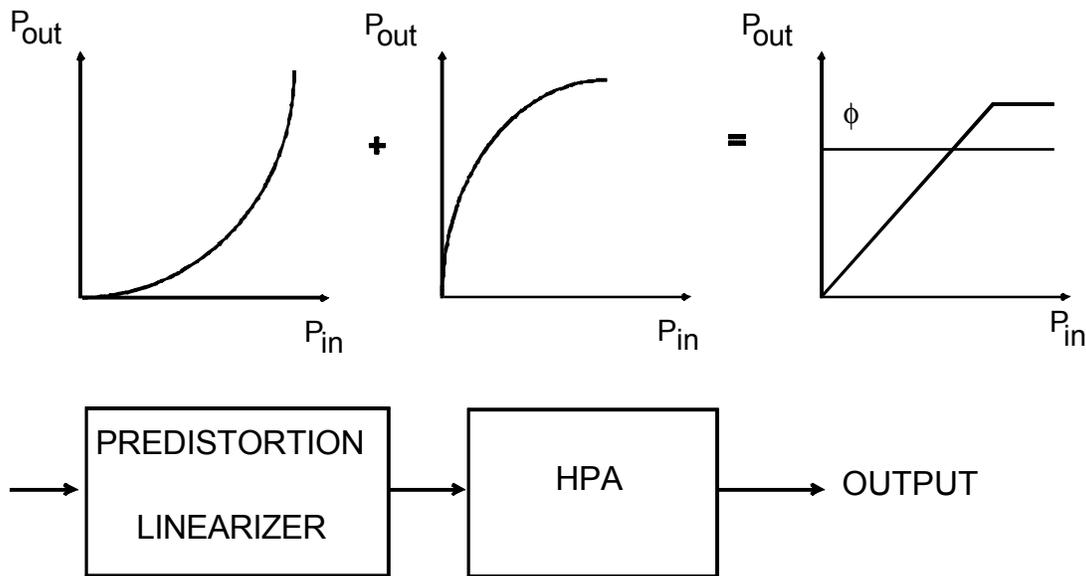▼ Figure 8:
 Predistortion linearizers generate a response opposite to an HPA's response in magnitude and phase



linearizer response needed to correct a given amplifiers transfer response. Figure 9 shows the response needed to ideally correct a typical TWTA. As SAT is approached the rate of gain and phase change become infinite.

$$dGL/dP_{in}=\infty \text{ and } d\Phi/dP_{in}=\infty \text{ as } P_{out} \rightarrow Sat.$$

Such a characteristic cannot be achieved in practice. Often a small amount of gain **expansion** near saturation due to the finite dGL/dP_{in} available is traded for superior C/I near SAT at the expenses of degraded C/I at higher OPBOs.

Another limitation of PD (and FF) is the dependence of some amplifier's transfer characteristic's on the frequency content of the signal. This phenomenon is sometimes referred to as *memory effects*. Great care must be taken in the design of an amplifier to minimize these effects, if the maximum benefit of PD linearization is to be achieved.

The 2-tone C/I achievable by an ideal transfer characteristic is shown in Figure 10. The C/I goes to infinity for OPBO greater than 3 dB. This result occurs because the peak-envelope-power (PEP) of a 2-tone signal is 3 dB greater than the average power. A signal backed-off by more than 3 dB never experiences clipping at SAT, and is subject to only a linear response. However, achieving this same level of performance

with a larger number of carriers requires a greater level of OPBO. This is a consequence of the increase in PEP with carrier number:


$$PEP=NP_{av}, \tag{19}$$

where N is the number of carriers and P_{av} is the average power of the overall signal. For 4 carriers the OPBO for no IMD increases to 6 dB.

The C/I for an ideal limiter driven by an infinite number of carriers (of random phase) is also show in Figure 10. The infinite carrier case is also known as noise power ratio (NPR). Although the OPBO required for a given C/I increases with N, the improvement provided by PD linearization also increases with N.

A PD linearizer can be produced by dividing an input signal into two parallel signal paths. One path is linear and can simply be a length of transmission line. The other path is nonlinear with a compression characteristic. This characteristic can be obtained from an amplifier driven into SAT. Subtracting the output signals from the two parallel paths results in a gain expansion (Figure 11)

$$V_{out}=V_{lin}-V_{nl} \tag{20}$$

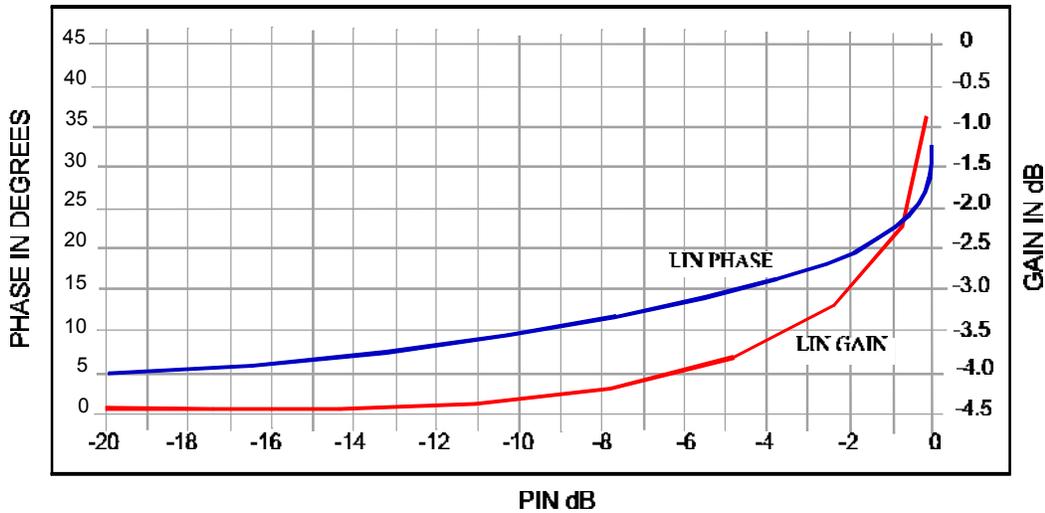


▲ Figure 9: An ideal PD linearizer response requires the gain and phase slope to become infinite as SAT is approached

The gain of the linear path (V_{lin}) remains constant with increasing drive level, while the gain of the non-linear path (V_{nl}) decreases as SAT is approached. Thus the overall gain (V_{out}) increases. Adjustment of the angle (θ) between the two paths allows the change of phase with level to be controlled.

Design advances have greatly simplified PD linearizers. Past linearizers were limited in bandwidth and dynamic range, and difficult to adjust. New designs can offer greater than octave frequency performance, and the complex non-monotonic transfer responses needed by some SSPAs. They are much smaller in size and provide enhanced performance with easy alignment and excellent stability.

Advances in digital signal processing (DSP) have caused great interest in synthesizing PD transfer characteristics digitally. Such systems offer the potential of the creating complex curves not readily produced by analog means. DSP PD's principal limitation is that processing must be done at base-band - requiring up and down conversion for use with a microwave amplifier. Correction Bandwidth (CBW) is also limited by the speed of the digital processor. The time between signal sampling is related not just to the signal BW, but also the number (N) of the signal BWs on either side of the signal where distortion reduction is required. Table I shows a summary of some of the advantages and disadvantages of DSP-based PD. A DSP-linearization system employing Cartesian predistortion

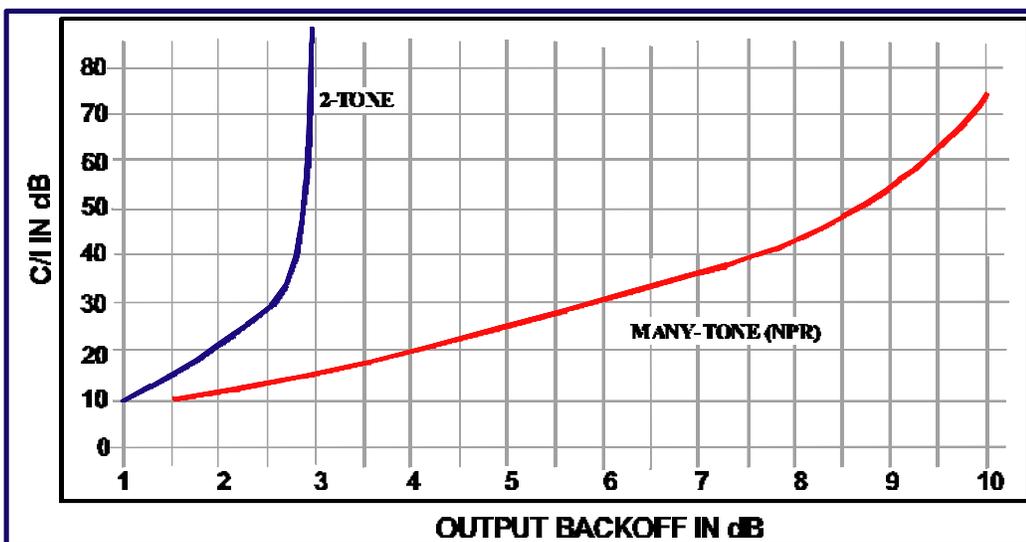

▲ Figure 10: C/I of an ideal linearizer for 2 and an infinite number of carriers (NPR)

and adaptive correction is illustrated in Figure 12. Today, speeds adequate for many personal-communications applications are achievable. In the near future, CBWs of several-hundred MHz will be practical.

Adaptive Linearization

For high linearity applications ($C/I > 50$ dB) adjustment and maintenance of optimal linearizer settings become very critical. A change in phase of less than a degree can move a linearized amplifier out of specification. As a result of this parameter sensitivity, much effort has been devoted to the development of linearizers that can automatically adapt to environmental and stimulus changes. DSP based linearization is particularly suitable for an adaptive approach.

Adaptive linearizers can be considered a form of IFB linearization in which the feedback is applied to PD and FF linearizers. A measure of the linearizer's performance is generated. This performance measure (V_{PM}) can take many forms but is always based on measurements over a time period greater than $2/BW$. V_{PM} can be derived from the difference between input and output waveforms (Figure 6) or the integrated IMD present in an unoccupied portion of spectrum near the desired signal. A microcomputer is normally used to analyze V_{pm} and determine the optimum linearized settings. In a FF linearizer, the microcomputer could to control A_0 and Φ_0 in the signal loop and A_1 and Φ_1 in the cancellation loop - see respective equations (9) and (10), and Figure 4. Using a search algorithm the computer would vary these parameters so as to

keep V_{pm} at a minimum value. Adaptive correction is particularly important in FF systems as the balance is only correct for a specific power level.

In the PD linearizer of Figure 11, the microcomputer could control the attenuator and phase shifter to maintain V_{pm} at a minimum value as in the FF example. Alternately, the desired non-linearity could be produced using a power series:



$$V_{out} = k_1 V_{in} + k_2 V_{in}^2 + k_3 V_{in}^3 \tag{21}$$

V_{in}^2 and V_{in}^3 can be generated using double balanced mixers. V_{in} is applied to both ports of the mixer to obtain an output of V_{in}^2 . A second mixer is used to obtain to V_{in}^3 . If needed, additional mixers can be used to obtain even higher powers. The values of coefficients k_1 , k_2 and k_3 could be controlled by the microcomputer. Two non-linear PD elements can be combined in an arrangement similar to a Cartesian feedback system to keep both gain and phase optimal.


These adaptive linearizers do not have the frequency response limitations of feedback linearizers, since they do not attempt to correct for changes in the signal's envelope. These linearizers respond slowly to gradual changes in the systems characteristics. Their principal disadvantage is complexity.

LINEARIZER ADVANTAGE

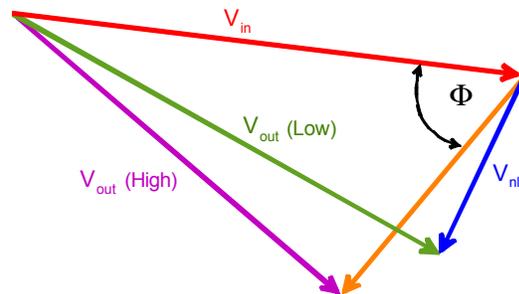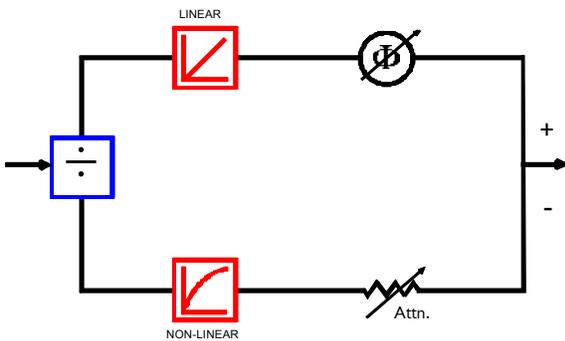The transfer characteristics of a typical TWTA and the corrected response provided by a contemporary predistortion lin-



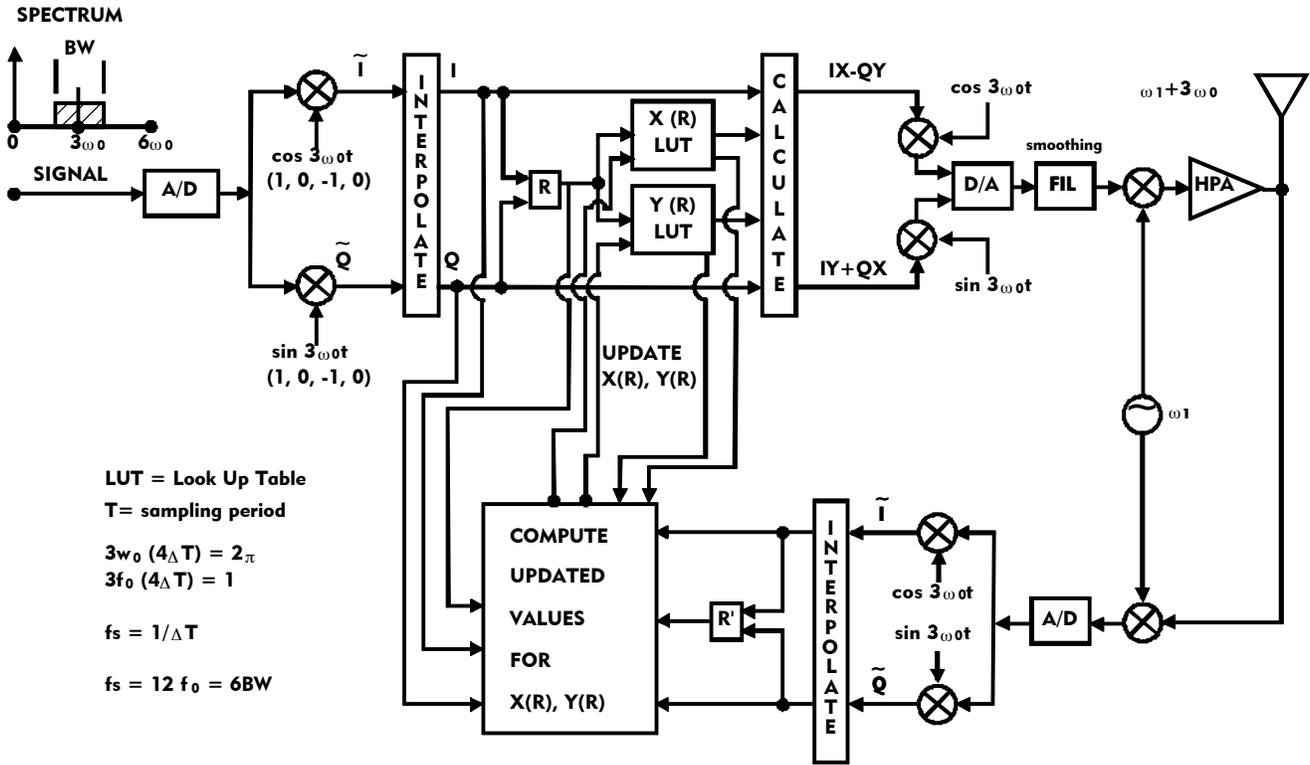
▲ Figure 11: Gain expansion can be produced by subtracting a linear path from a non-linear path




▲ Figure 12: DSP linearization system using Cartesian predistortion and adaptive correction

erizer are shown in Figure 13. Note how the shape of the linearized P_{out}/P_{in} curve approaches the desired ideal limiter characteristic of Figure 8. The separation of the 1 dB CP from SAT is a good indicator of linearizer performance. Ideally the

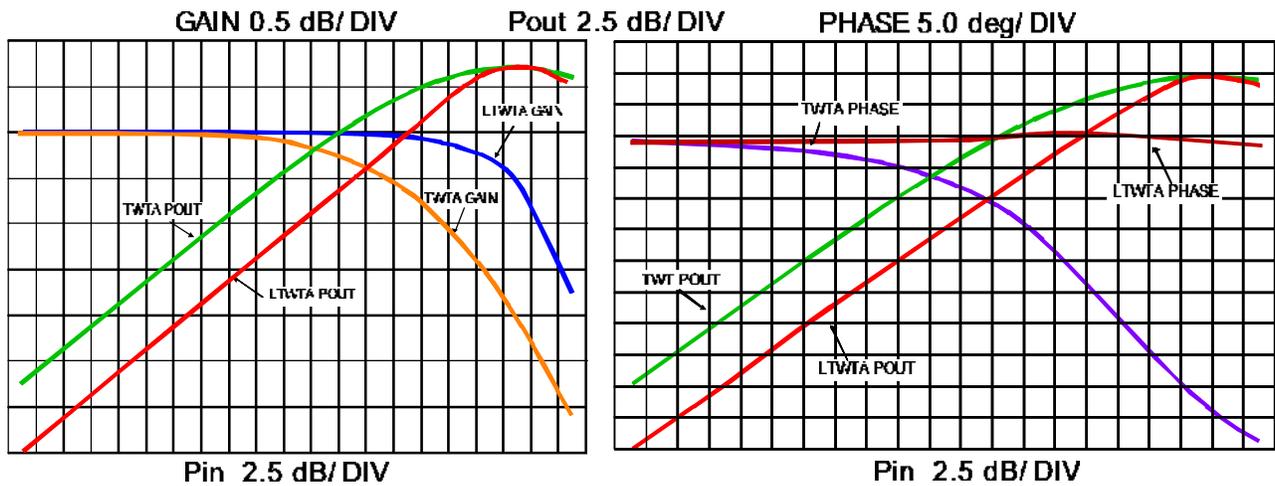1 dB CP is located 1 dB in input power beyond SAT. It is not unusual for TWTAs to have the 1 dB CP occur 10 to 12 dB before saturation. In Figure 13 the 1 dB CP is moved from 6.25 dB before SAT for the TWTA, to just about SAT for the linearized TWTA. The linearizer also reduces the change in



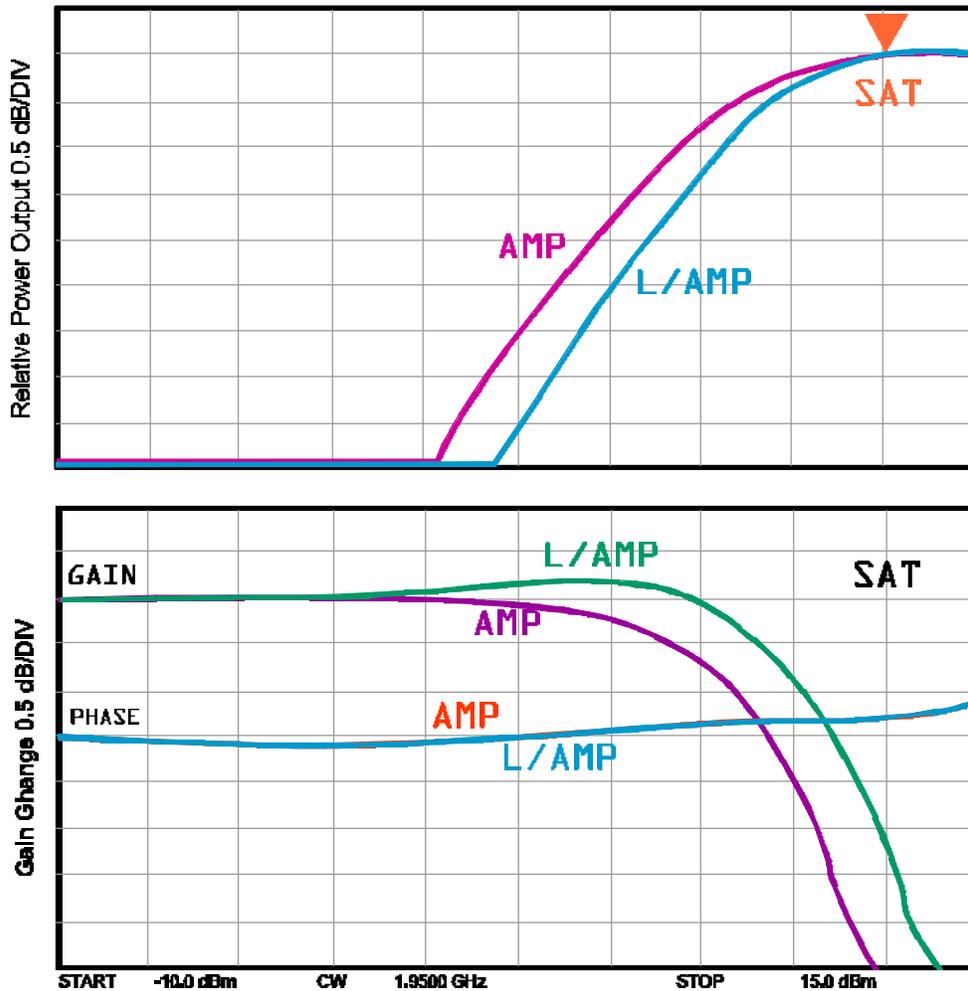▲ Figure 13: Transfer characteristics of TWTA and linearized TWTA



▲ Figure 14:
Transfer characteristics of a class A S-band SSPA and linearized SSPA

phase with power level from more than 40 degrees for the TWTA alone to a near flat line.


Figure 14 shows the transfer characteristics of a SSPA and the corresponding corrected response resulting from linearization. The characteristics are for a class A power MESFET amplifier.

Although the change in 1 dB CP is not as great as for a TWTA, the benefit can still be substantial.


An example of the two-tone output spectrum of a typical TWTA with and without linearization at 4-dB OPBO, is shown in Figure 15. A reduction in IMD of greater than 15 dB is common at this OPBO level. The improvement in two-tone C/I as a function of OPBO achieved by using a PD linearizer with

a TWTA, a class A MESFET SSPA and a class AB MESFET SSPA are depicted in Figures 16, 17 and 18 respectively. For a TWTA at a C/I of 26 dB, the linearizer can provide a greater than 3 dB increase in output power. If a C/I ratio of 30 dB is required, the TWTA would have to be backed off at least 10 dB, but with the linearizer, it need only be backed-off 4 dB. This is a 6 dB increase in output power.

The advantage of linearizing SSPAs varies greatly with bias class and device type. The class A amplifier of Figure 17 shows only about a 0.5 dB increase in output power for a C/I of 26 dB, but a 2.5 dB power increase for a 50 dB C/I. The class AB SSPA, Figure 18, shows about a 1.5 dB increase in output power for a C/I of 26 dB. Ordinarily the more linear an SSPA, the less the advantage of linearization. When designing an

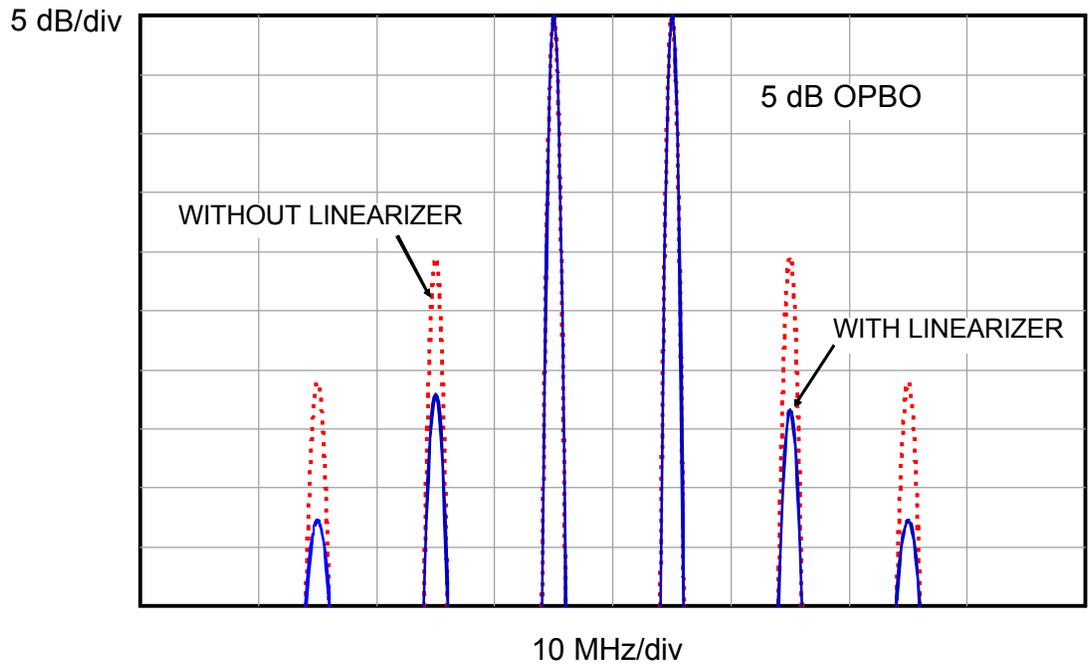

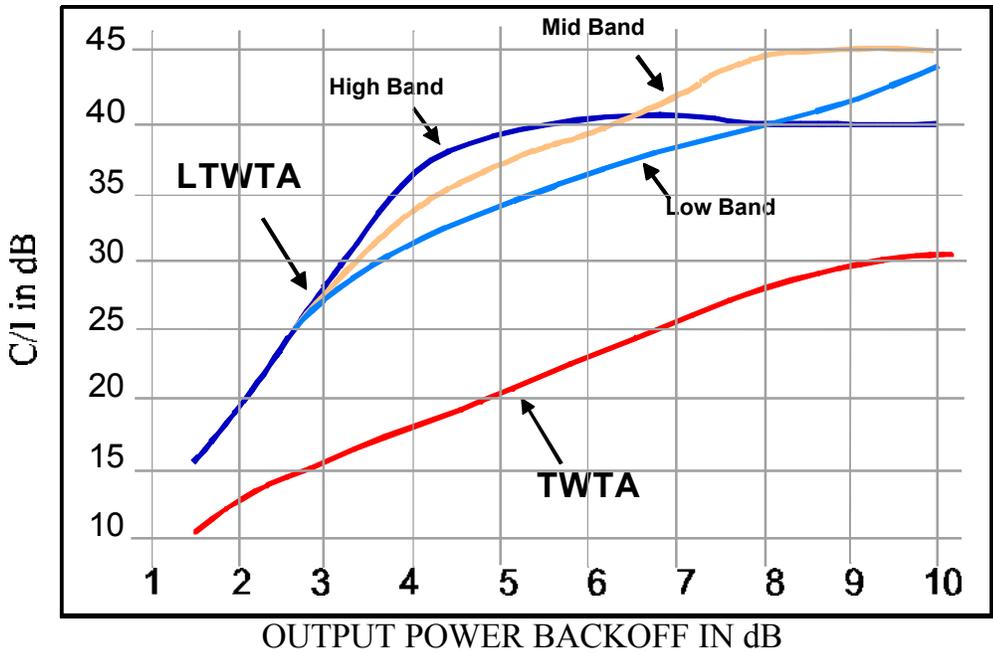▲ Figure 15:
 For a TWTA, a 2-tone C/I improvement of
 > 15 dB at 4 dB OPBO is Common




◀ Figure 16:
 A 4 x increase in
 power for a 2-tone
 C/I of 30 dB can be
 obtained by lin-
 earizing a TWTA

HPA to be linearized, emphasis should be placed on optimizing factors other than linearity.


An even greater HPA output power increase should be achieved for signals of more than 2 carriers, although a higher level of OPBO will be required for the same C/I level as the number of carriers is increased. Generally the greater the lin-

earity requirement, the greater the benefit of using a linearizer. Conversely the closer an HPA is operated to SAT, the smaller the benefit of using a linearizer.

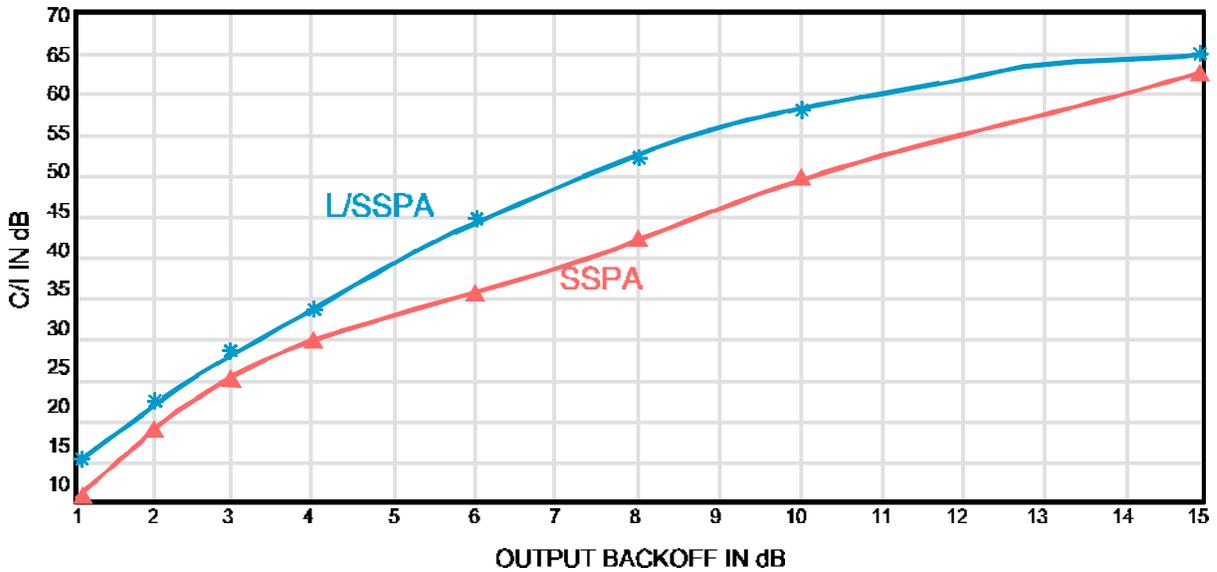
There can be other reasons, besides increased output power, for linearizing an HPA. For example thermal considerations can place major constraints on the design of an HPA. Linearization increases an HPA's efficiency by allowing it to



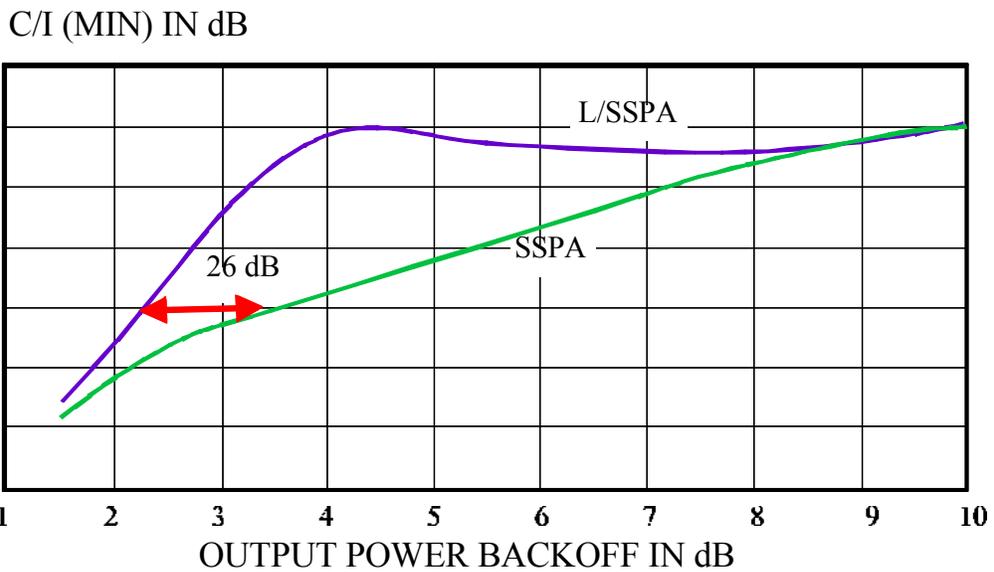▲ Figure 17:
Linearizing a class A SSPA gives only 0.5 dB more power at 26 dB C/I, but 2.5 dB at a 50 dB C/I



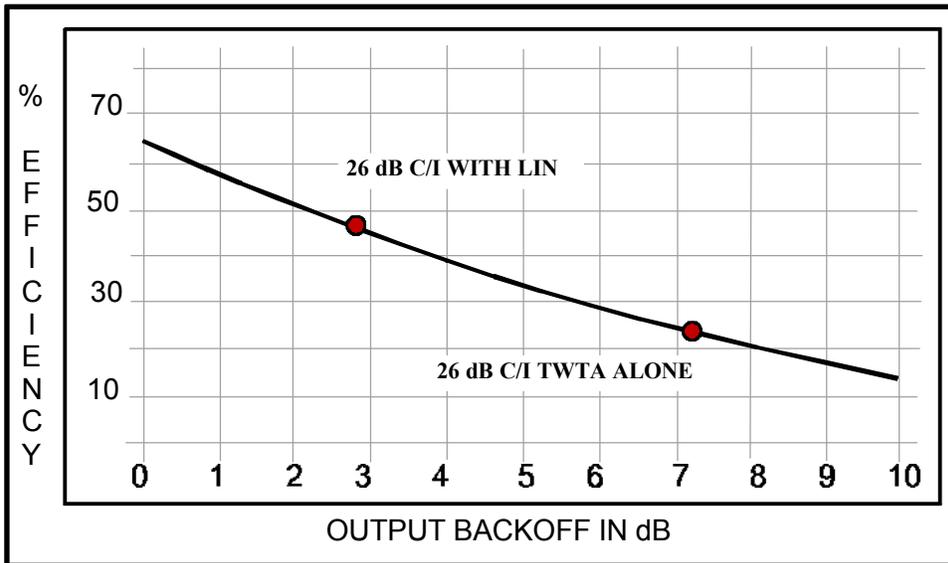▲ Figure 18:
Linearizing a less linear class AB SSPA gives >1.5 dB more power at a C/I of 26 dB




▲ Figure 19. A very significant increase in TWTA efficiency can be achieved for a C/I of 26 dB

operate closer to SAT. Increased efficiency reduces thermal loading. Figure 19 shows how efficiency is related to OPBO for a modern high efficiency TWTA. For a C/I of 26 dB, the use of a linearizer can provide greater than a 70 percent efficiency increase. In the case of an SSPA, linearization may allow operation at a more efficient bias than would have been otherwise possible.


The performance of a linearized HPA with many carriers (>10) is normally tested using a noise power ratio (NPR) measurement. In this test white noise is used to simulate the presence of many carriers of random amplitude and phase.

The NPR of a typical TWTA and a linearized TWTA are shown in Figure 20. In Figure 21 similar NPR measurements are shown for a class AB SSPA.

With single carrier modulated signals, a linearizer can often be of great value, especially with BEM. For example, HPAs transmitting single carrier quadrature phase-shift-keyed (QPSK) and offset QPSK (OQPSK) signals are usually operated at a reduced output level. They are backed-off to prevent SR, which can interfere with adjacent channel signals. Linearization can reduce this spreading to an acceptable level (> 25 dB) for OPBOs of 0.25 to 0.5 dB from saturation. Figure 22 shows an

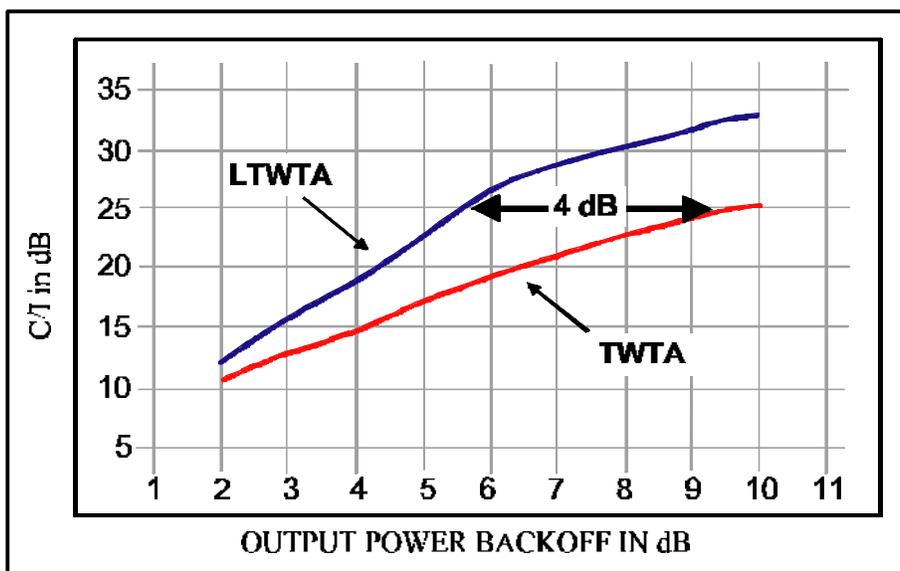

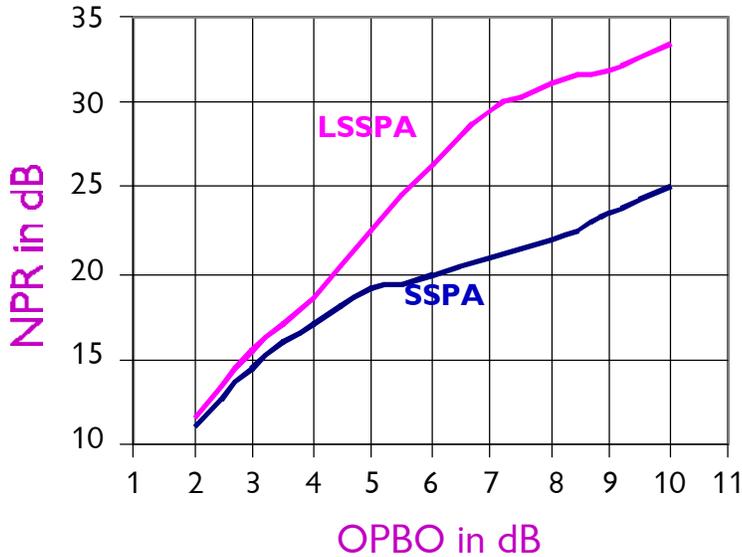
◀ Figure 20: NPR predicts amplifier performance with many carriers. NPR is for TWTA




◀ Figure 21:
NPR of class AB SSPA

illustration of the improvement provided by a linearizer for a QPSK (or OQPSK) satellite signal. At 4 dB OPBO about a 10 dB decrease in interference level is achieved. Figure 23 shows the reduction in spectral regrowth achieved by linearization of a TWTA. It has been found empirically that a 30 dB SR corresponds to a 2-tone C/I ratio of about 25 dB. The SR of QPSK and OQPSK modulation are similar adjacent to the modula-

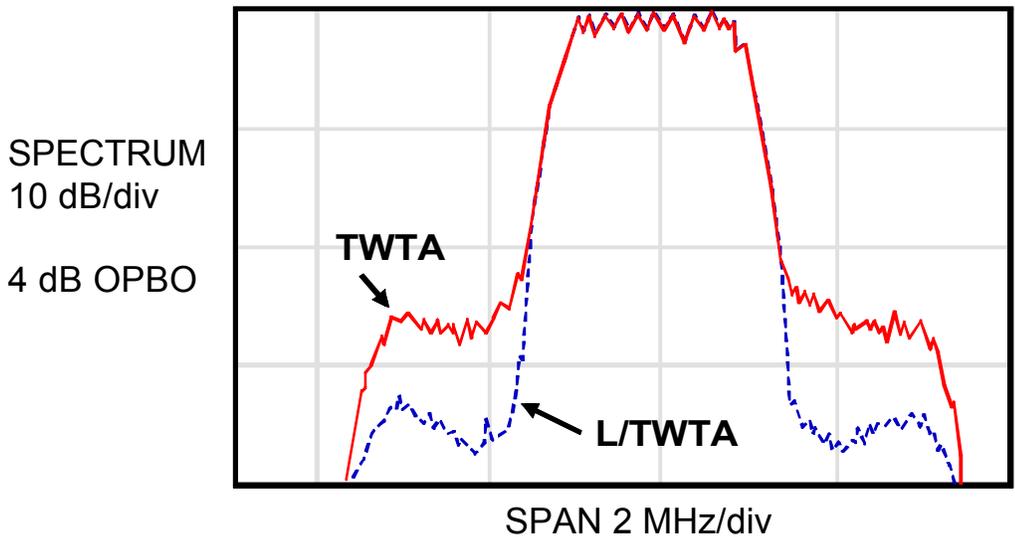tion bandwidth; however, OQPSK gives improved SR performance at greater frequency separation. Generally the SR of binary phase-shift-keyed (BPSK) and 8PSK are close to that of QPSK/ OQPSK with BPSK having slightly poorer (~1 dB) and 8PSK providing slightly better performance (~1 dB). In most cases linearization can also improve the bit-error-rate (BER) of digital modulated signals.



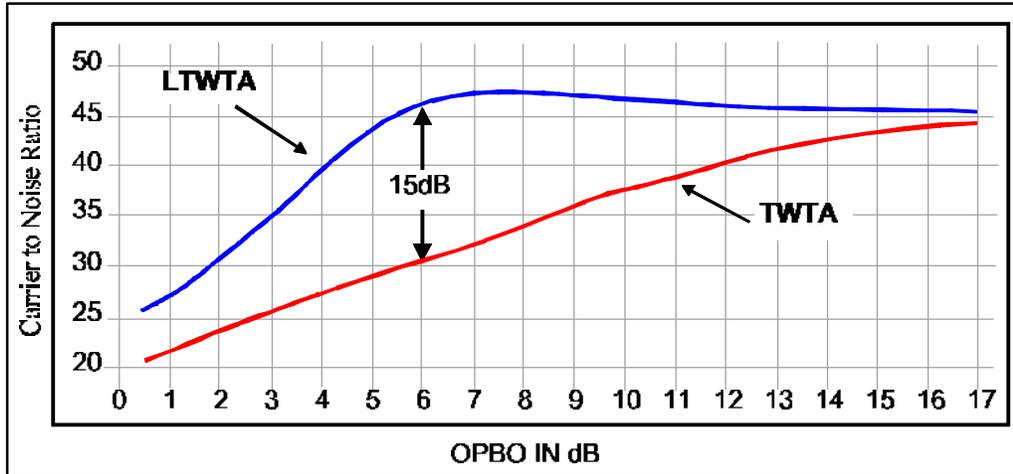◀ Figure 22:
Bandwidth/noise reduction of QPSK signal achieved by linearization



▲ Figure 23:
Reduction in spectral regrowth provided by linearization of a TWTA

SUMMARY

Linearizers are needed to increase HPAs' power capacity and efficiency when handling multi-carrier and BEM traffic. New linearizer designs have greatly enhanced performance and bandwidths, made alignment easier, and provide excellent stability and reliability. These linearizers can deliver up to a 4-fold increase in TWTA power capacity, and more than double TWTA efficiency. They can increase SSPA power capacity and efficiency when high linearity is required. The greatest benefit is accrued for class B and AB amplifiers in applications requiring a high linearity. In these cases, linearizers can deliver a greater than 3 dB increase in power capacity, and more than double SSPA efficiency. Generally feed-forward and adaptive linearization are most valuable for applications requiring very high linearity. Indirect feedback methods work well, but are limited in bandwidth. Predistortion has the advantage of relative simplicity. It works over wide bandwidths and is viable for applications requiring both low and moderate linearity.

REFERENCES

- [1] J. Balicki, E. Cook, R. Heidt, and V. Rutter, "The AR6A Single-Sideband Microwave Radio System: The Traveling Tube Amplifier," *bell syst tech J.*, Vol. 62, No. 10, pp. 3429-3445, Dec. 1983.
- [2] E. Ballesteros, and F. Perez. "Microwave Power Amplifiers Linearized By Active Feedback Networks," presented at the IEEE MTT-S Symp. Workshop on Linearizers, June 1988.
- [3] W. Bosch and G. Gatti, "Measurement and simulation of memory effects in predistortion linearizers," *IEEE Trans. Microwave Theory Tech.*, vol. 37, pp. 1885-1890, Dec. 1989
- [4] C. Bremenson, et al., "Linearizing TWT amplifiers in satellite transponders, systems aspects and practical implementation." in *Proc. AIAA 8th Communication Satellite Systems Conf.*, pp. 80-89.
- [5] D. Cahana, et al., "Linearized Transponder Technology for Satellite Communication, Part I: Linearizer circuit development and experimental characterization," *COMSAT Tech. Rev.*, Vol. 15, No. 2A, pp. 277-308, Fall 1985.
- [6] R. Inada, et al., "A compact 4-GHz linearizer for space use,"

IEEE Trans. Microwave Theory Tech., vol. 34, pp. 1327-1332, Dec. 1986.

[7] A. Katz and R. Dorval, "Evaluation and correction of time dependent amplifier non-linearity," *IEEE MTT-S IMS Dig.*, pp. 839-842, Jun. 1996.

[8] A. Katz et al., "A reflective diode linearizer for spacecraft applications," *IEEE MTT-S IMS Dig.*, pp. 661-664, Jun. 1985

[9] P. Kenington, "Methods linearize RF transmitters and power amps, part I," *Microw. RF*, pp. 103-116, Dec. 1998.

[10] P. Kenington, "Methods linearize RF transmitters and power amps, part I," *Microw. RF*, pp. 79-89, Jan. 1998.

[11] A. M. Khilla, et al, "Multi-band predistortion linearizers for satellite transponders and ground stations," *AIAA J.*, pp. 927-937, 1992.

[12] Y. Lee, I. Brelian, and A. Atia, "Linearized transponder technology for satellite communications; Part 2: System simulation and performance assessment," *COMSAT Tech. Rev.*, Vol. 15, No. 2A, pp. 309-341, Fall 1985.

[13] M. Kumar, et al., "Predistortion linearizer using GaAs dual-gate MESFET for TWTA and SSPA Used in satellite transponders," *IEEE Trans. Microwave Theory Tech.*, vol. 33, pp. 1479-1484, Dec 1985.

[14] J. Minkoffm "Intermodulation noise in solid-state Power Amplifiers for Wideband Signal Transmission," *Proc. AIAA 9th Com. Satellite Sys. Conference*, 1982.

[15] S. Moochalla, et al., "An Integrated Ku-band linearizer driver amplifier for TWTAs with gain and wide bandwidth," presented at the AIAA 14Th Int. Communications Satellite Systems Conf., 1992.

[16] A. Saleh, "Intermodulation analysis of FDMA satellite systems employing compensated and uncompensated TWTs," *IEEE Trans. Commun.*, vol. 30, no. 5, pp. 1233-1242, May 1982.

[17] G. Satoh and T. Mizuno, "Impact of a new TWTA linearizer upon QPSK/TDMA transmission performance." *IEEE J. Select. Areas in Commun*, vol.1, pp.39-45, Jan. 1983.

[18] J. Steck and D. Pham. "A new TWT linearizer for satellite-communications transmitters," *Microw. Syst. News Commun. Tech.*, vol.17, no.9, pp.28-42, Jun. 1987.